

D 029

B.E./B.Tech. DEGREE EXAMINATION, APRIL/MAY 2003.

Third Semester

Electronics and Communication Engineering

EC 231 — NETWORK ANALYSIS AND SYNTHESIS

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Define Ideal Voltage Source.
2. For a capacitor with initial voltage $v_c(0^-)$, write down the expressions for current and voltage in S-domain.
3. A series network consists of a resistor $R = 1 \Omega$ and a capacitor $C = 0.05 \mu F$. Write down the expression for magnitude and phase response with respect to frequency.
4. A series RC circuit is excited by a voltage source $v(t)$ at time $t = 0$. Write down the state space equation.
5. Define 'positive real function'.
6. List four important properties of a driving point impedance function of an RC network.
7. Compare Butterworth and Chebyshev approximations.
8. With an example, illustrate voltage controlled voltage source.
9. Find the Z-parameters of a T-network having 1 H series arm impedances and 0.5 F shunt arm capacitance.

10. Draw the circuit diagram of a second order single OP-AMP Sallen-Key low pass filter.

PART B — (5 × 16 = 80 marks)

11. Derive the state space equations of a second order RLC series circuit excited by a voltage source $v(t)$. If the parameter matrix A has the elements $A_{11} = -2$, $A_{12} = 1$, $A_{21} = 0$, $A_{22} = -1$, find the state transition matrix.
12. (a) For the network shown in Figure 12.a, find the current $i_2(t)$. The network is deenergised before $t = 0$.

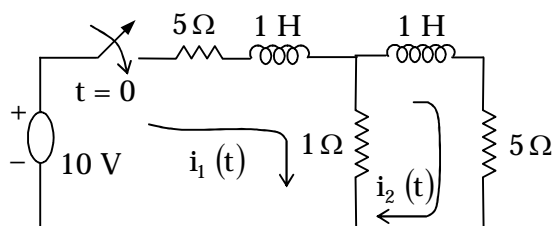


Figure 12.a

Or

- (b) For the resistive network shown in Figure 12.b, draw a graph, select a tree and obtain tie-set matrix. Write down the KVL equations from the tie-set matrix.

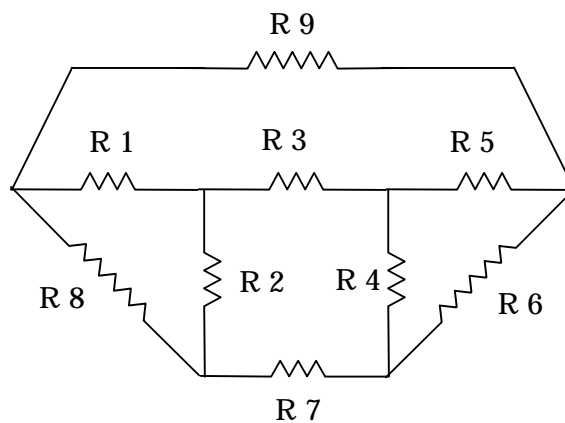


Figure 12.b

13. (a) Realise the function $F(S) = \frac{(S^2 + 1)}{S(S^2 + 2)}$ in Foster form I.

Or

- (b) For the function $Z(S) = \frac{(S^2 + 1)(S^2 + 9)}{S(S^2 + 4)}$. Obtain Cauer form II.
14. (a) Obtain the transfer function of a Butterworth lowpass filter for the following specifications :
- (i) Cutoff frequency $\omega_c = 0.75$ rad/sec.
 - (ii) Amplitude is 20 dB down at $\omega = 3$ rad/sec.

Or

- (b) Design a normalised second order Butterworth high pass filter by frequency transformation and plot the approximate magnitude response.
15. (a) (i) What are the advantages of active filters over passive filters?
- (ii) Describe the principle of operation of an active second order high pass filter.

Or

- (b) Describe the principles of design of an active low pass filter.
- _____