

M 077

MODEL PAPER

B.E. DEGREE EXAMINATION.

Fourth Semester

Electrical and Electronics Engineering

EC 254 — ELECTRONIC CIRCUITS


Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. With the small signal equivalent circuit, define the parameters of a JFET.
2. Draw the circuit diagram of a Darlington Emitter follower. What are the advantages of this amplifier?
3. What are the advantages of using FET input stages?
4. Draw a single tuned amplifier circuit diagram and its frequency response characteristics.
5. With a block diagram, obtain the closed loop transfer gain of a feedback system.
6. Draw the circuit of a Wien Bridge Oscillator.
7. Sketch the output waveform of a Schmitt Trigger with $UTP = 5\text{ V}$ and $LTP = 3\text{ V}$ for a 12 V peak to peak 1 kHz sinewave input.
8. Why the RC circuit given in fig. 1 is called a High Pass filter?

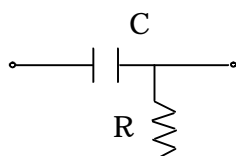

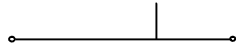


Fig. 1

9. Draw the circuit schematic of a simple 3 phase Half Wave Rectifier.
10. Give a functional block diagram of a switched Mode Voltage Regulators.

PART B — (5 × 16 = 80 marks)

11. With differential mode and common mode small signal equivalent circuits, calculate CMRR for the differential amplifier with double ended output having the following specifications :

$$R_C = 1 \text{ k}\Omega, R_{EE} = 10 \text{ k}\Omega, h_{ie} = 1 \text{ k}\Omega, h_{fe} = 200, h_{re} = h_{oe} = 0.$$

12. (a) Using Miller's theorem, calculate A_V , A_{VS} , R_{in} and R_o of the Common Emitter amplifier shown in fig. 2.

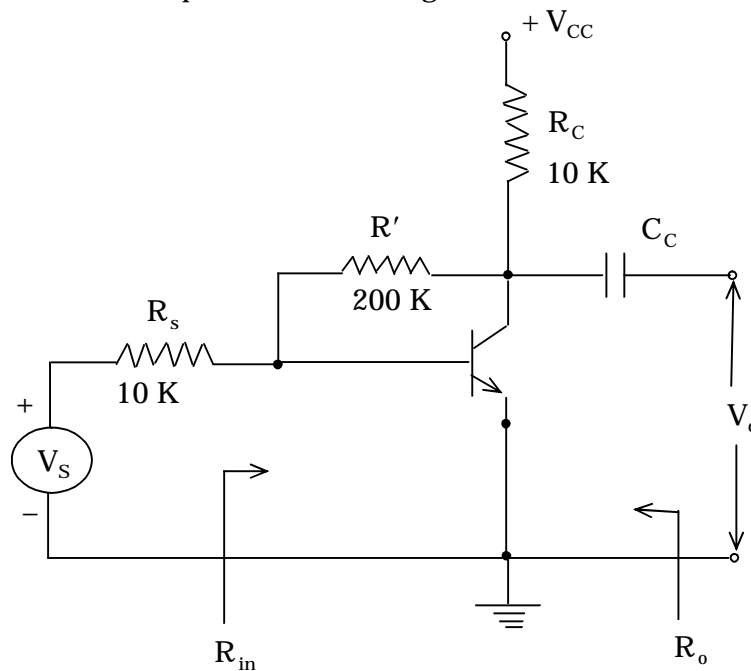


Fig. 2

The BJT has the following parameters :

$$h_{ie} = 1.1 \text{ k}\Omega$$

$$h_{fe} = 50$$

$$\frac{1}{h_{oe}} = 40 \text{ k}\Omega$$

$h_{re} = 0.$

Or

- (b) (i) With a suitable circuit diagram and waveforms, explain the operation of a class B power amplifier using complementary symmetry transistors. (12)
 - (ii) Draw the circuit diagram of a class C power amplifier. Indicate the base and collector voltage waveforms. (4)
13. (a) (i) Derive R_{if} and R_{of} of a voltage series feedback amplifier. (8)
- (ii) Compare the frequency response characteristics of an amplifier with and without feedback. (4)
 - (iii) Draw the circuits of single stage voltage series and current series feedback amplifiers. (4)

Or

- (b) (i) Draw the circuit of a transistor Hartley Oscillator. Obtain the frequency of oscillation. (12)
 - (ii) What are the advantages of crystal oscillators? Draw a crystal oscillator circuit. (4)
14. (a) Design and draw a Monostable Multivibrator for the following specifications :
- $V_{CC} = 12\text{ V}; V_{BB} = 6\text{ V}; I_{C(on)} = 1\text{ mA};$
- duration of output pulse 10 m seconds;
- $h_{FEmin} = 100; I_{CBO} \approx 0, V_{BE(off)} = -0.5\text{ V}.$

Or

- (b) (i) With circuit diagram and output voltage waveform, derive an expression for the period of oscillation of a UJT relaxation oscillator. (10)
- (ii) Sketch the output waveforms of the following non linear RC wave shaping circuits given in fig. 3 and fig. 4. (6)

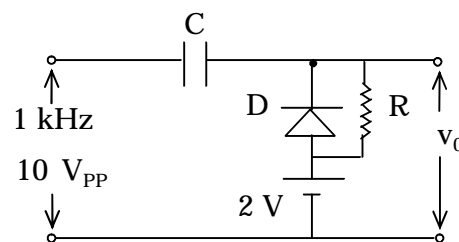
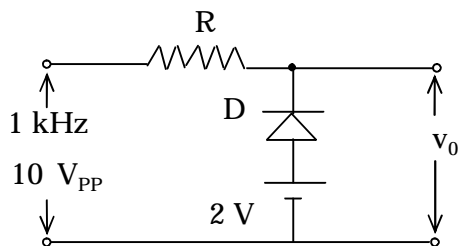


Fig. 3

Fig. 4

15. (a) With circuit diagram explain the operation of a transistor series voltage regulator with short circuit overload protection and current preregulation.

Or

- (b) (i) Obtain an expression for the ripple factor of a capacitor input (RC) filter that follows a full wave rectifier, using the voltage waveforms. (10)
- (ii) Show that the maximum rectification efficiency η_R of a full wave rectifier is 81%. (6)

—————